

## Voltage in Series & Parallel Circuits

**Purpose:** to compare the voltage of batteries (cells) in series and parallel circuits

**Materials:** 4 batteries, voltmeter, wire with alligator clips

### Procedure and Data:

#### Part I – Measuring Voltage

1. Obtain and record the voltage of 4 different cells (batteries a, b, c, d)

Battery	A	B	C	D
Voltage				

#### Part II – Voltage in Circuits

1. Draw the circuit diagrams for:

a) Series circuits

1 Battery

2 Batteries

3 Batteries

4 Batteries

b) Parallel circuits

1 Battery

2 Batteries

3 Batteries

4 Batteries

2. Measure the voltage of each circuit described below

Circuit Type	# of Batteries	Voltage (V)
-----	1	
Series	2	
Series	3	
Series	4	
Parallel	2	
Parallel	3	
Parallel	4	

**Conclusion:**

1. Why did your batteries not have the same voltage when you measured them in part I?

2. What happens to the total voltage of a circuit when you add batteries in series?

3. What happens to the total voltage of a circuit when you add batteries in parallel?

Circle the best term in the parentheses to correctly complete each statement.

- A series circuit has (more than one, only one) path for current to travel.
- A parallel circuit has (only one, more than one) path for current to travel.

## Fruit Battery Experiment

**Purpose:** to compare the electrochemical potential energy of fruit (cells)

**Materials:** apple, banana, grapefruit, guava, lemon, lime, orange, voltmeter, alligator clips, screws

### Procedure and Data:

1. Obtain and record the voltage of the 7 different fruits.

Fruit	Apple	Banana	Grapefruit	Guava	Lemon	Lime	Orange
Voltage							

### Results

Order of fruit starting with the most voltage fruit measured on the voltmeter (MVF “most voltage fruit”)

- 1.
- 2.
- 3.
- 4.
- 5.
- 6.
- 7.

### Conclusion

1. What did you already know before doing this experiment?
2. Did this experiment make you wonder about anything?
3. What did you learn from this experiment?

## Lighting It Up Activity

**Purpose:** to light a bulb

**Materials:** D cell, wire with alligator clips, light bulb

### **Procedure and Data:**

1. Using the flashlight bulb, wire and battery, try to make the bulb light up. Once you are successful, disconnect the battery. Make a sketch of these three materials were connected.
2. Rearrange the three materials and find a different way to make the bulb light up. Make a sketch of this second circuit.
3. Make a sketch that includes the three objects in such a way that the bulb will not light up. Then, using the materials, check if your sketch is correct.

### **Conclusion**

1. Explain the difference between the sketches in steps 1 and 2 and the sketch in step 3.
2. Which of your sketches show a complete circuit
3. Give an example of something in your home or community that represents a complete circuit.