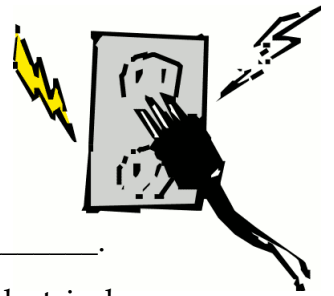


# CURRENT ELECTRICITY



- Static electricity forms when charges remain on an object for a while.
- Current electricity forms when \_\_\_\_\_.
- Current is formed when a device changes other forms of energy into electrical energy.

## CURRENT ELECTRICITY:


- Results from the \_\_\_\_\_ of
- The movement has TWO components:
  - A. \_\_\_\_\_ - **measured in Volts (v)** - similar to water pressure
  - B. \_\_\_\_\_ - **measured in Amperes (A)** - similar to water flow  
(how much water past a certain point in one second)

## VOLTAGE (V):


- To make electrons move, they have to be pushed. They are forced along a metal in one direction.
- This push is called voltage or \_\_\_\_\_.
- Measured in \_\_\_\_\_ by a device called a \_\_\_\_\_.
- It can be described as a measure of the electrical pressure produced by battery or power supply.

We get electrical energy from a \_\_\_\_\_.

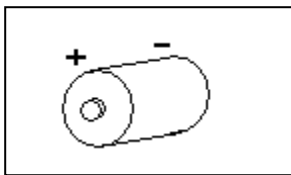Two or more chemical cells joined together is a \_\_\_\_\_.



Cell

 


(symbol in schematic diagrams)
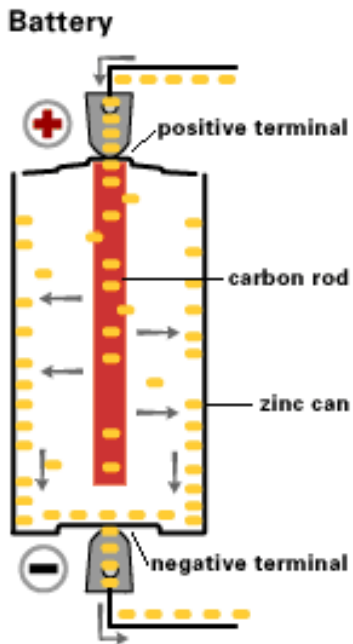
## BATTERIES:

Batteries produce a \_\_\_\_\_ by using \_\_\_\_\_ to produce a difference in electrical potential energy between the positive and negative terminals.

Electrons are pushed from the \_\_\_\_\_ terminal to the \_\_\_\_\_ terminal.




- ❖ The size of the \_\_\_\_\_ is called \_\_\_\_\_
- ❖ Electrons at the negative terminal are \_\_\_\_\_ and therefore have \_\_\_\_\_ (pressure) and want to get away from each other.

Batteries can be connected in **TWO** ways:


1) **SERIES:** \_\_\_\_\_.

Schematic Diagram:

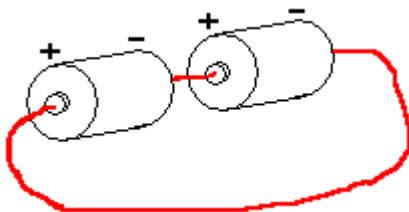

2) **PARALLEL:** \_\_\_\_\_.

Schematic Diagram:

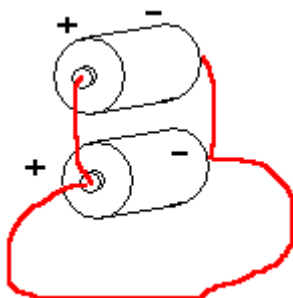

## SHORT CIRCUIT:

If a circuit is interrupted allowing a current to travel down an \_\_\_\_\_ path, it causes too much \_\_\_\_\_ in a wire. That is called a \_\_\_\_\_.

The excessive current can either cause the power source (like a \_\_\_\_\_) to heat up, “short” and be destroyed; or a \_\_\_\_\_ (if it is doing its job) to blow, breaking the flow of current in the circuit.

At home, a short circuit can be \_\_\_\_\_ and \_\_\_\_\_ to your appliances and electronic devices. The most common cause of a short circuit in the home is \_\_\_\_\_ touching when they shouldn't.

