


Circuit Design

Jaeda

Circuit 1. series circuit

must include: colour: white


2 lights
1 switch

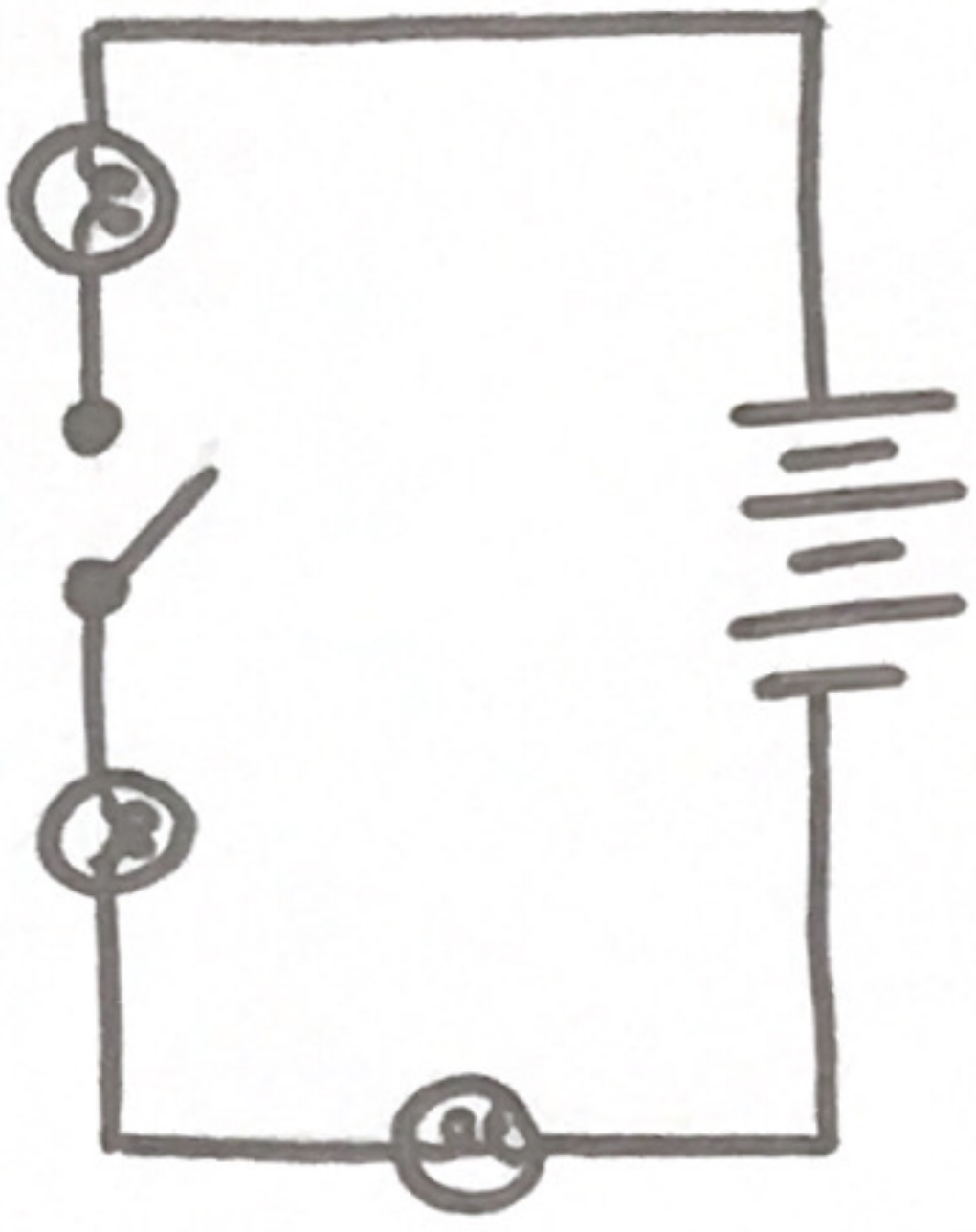

Circuit 3. combo circuit (S+P)

must include: colour: white


3 lights
2 switches

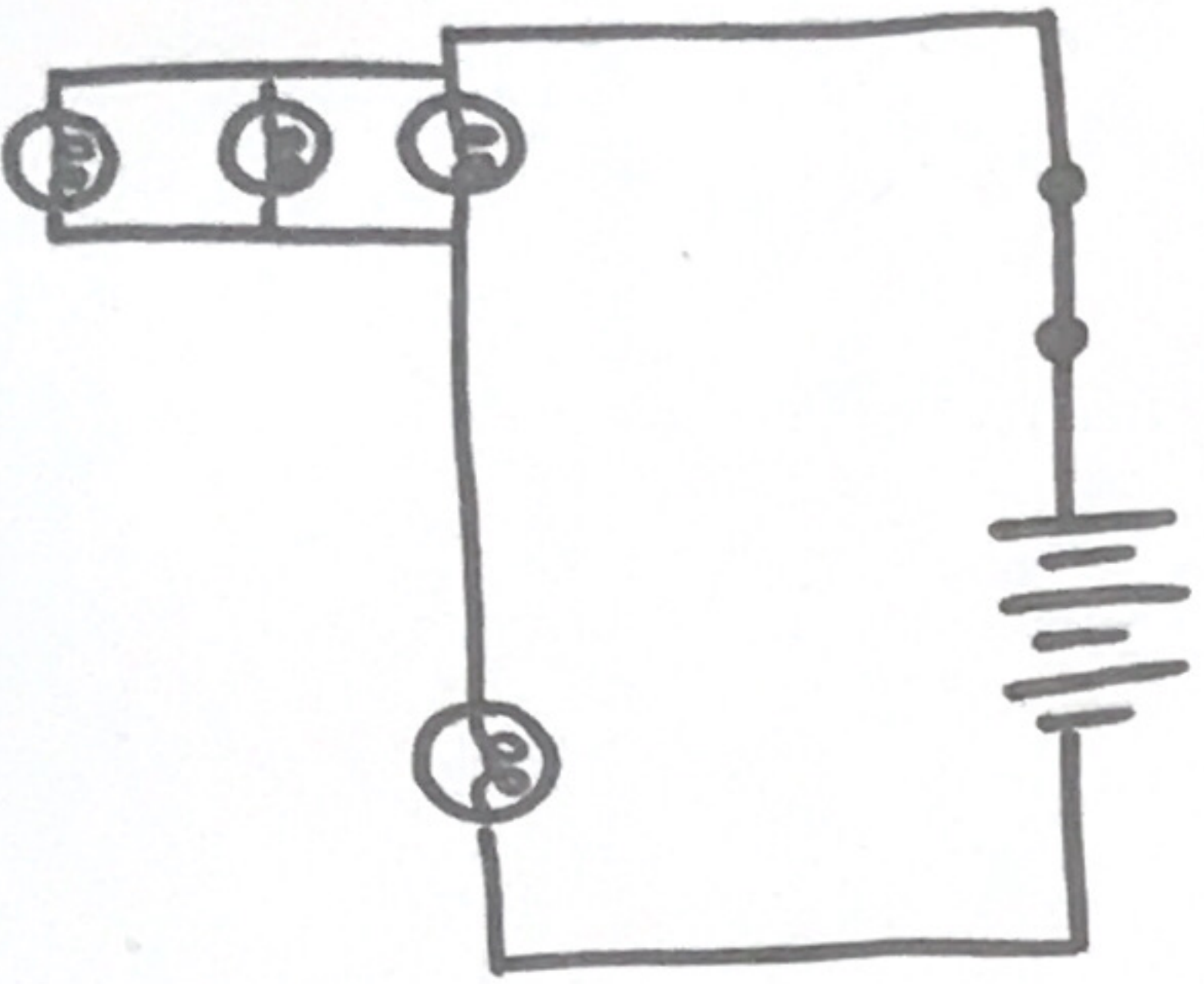

Circuit 2. parallel circuit

must include: colour: white

2 lights
1 switch

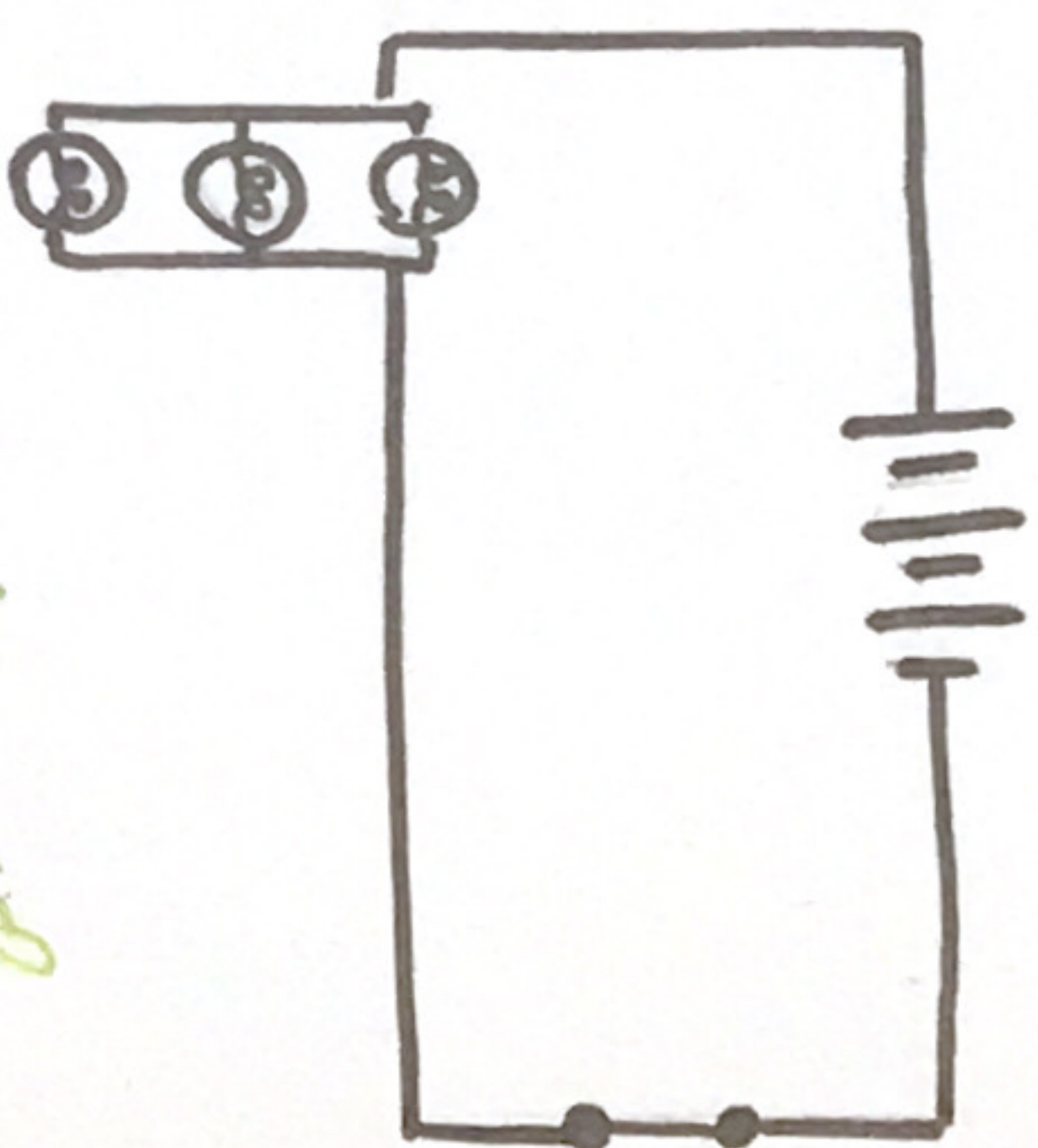

Circuit 4. choice circuit

must include colour: white

3 lights
2 switches

